

COMPUTER TECHNOLOGY

PRACTICAL SESSION P3

COMBINATIONAL CIRCUITS: SUB-CIRCUITS INTEGRATION

INTRODUCTION

The objective of this practical session is to design a digital circuit composed of three sub-circuits (see figure below). The input of the circuit is a 8-bit vector V, that is provided by an external source (the student freely provides this bit-vector).

- Subcircuit 1 visualizes the number of the highest active-high bit in V (highest priority)
- Subcircuit 2 implements function F, which takes value 1 if the number of the highest active-high bit of V is even, with the exception of number 0, in which F=0. Otherwise F=0.
- Subcircuit 3 implements function G, which takes value 1 if the number of 1's of the binary code of the number of the highest active-high bit of V is odd. Otherwise, $G=0$.

Figure 1 shows the main circuit and one example in which the 8-bit input is $V=00011110$. According to this input, the number of the highest active-high bit is 4. The display then visualizes 4. Since 4 is an even number, $F=1$. Finally, the binary code of 4 is 100, which contains one 1, which is an odd number, and, consequently, $G=1$.

The student must implement Subcircuits 1, 2 and 3 and, finally, implement the main circuit.

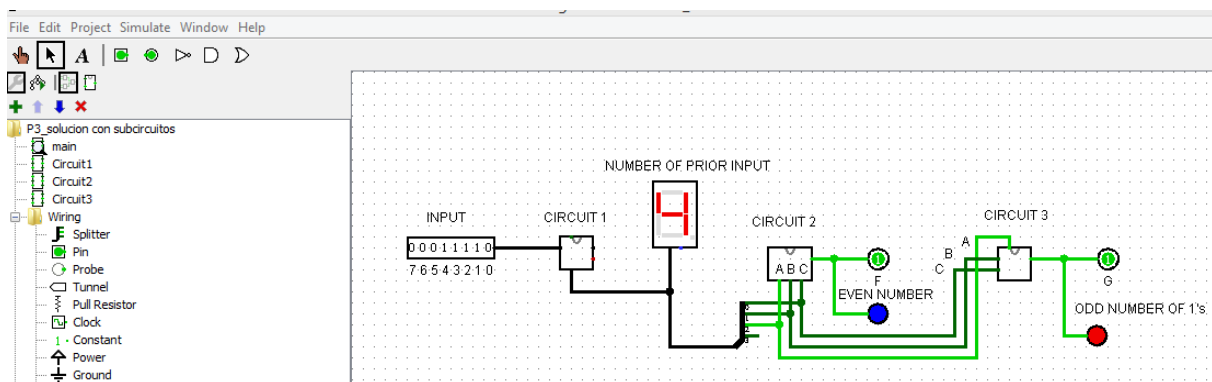


Figure 2

PART 1. Subcircuit 1

Design and implement subcircuit 1 using the following modules of Logisim:

- Priority Encoder
- Hex Digit Display, which visualizes a BCD number in a display.

Suggestions:

- Move the mouse pointer over the small dots of the modules (see figure below) in order to see and understand the meaning of the inputs and outputs.
- Use the Splitter (in the *Wiring* panel) to convert separate data to a databus (bit-vector) and vice versa.

COMPUTER TECHNOLOGY

PRACTICAL SESSION P3

COMBINATIONAL CIRCUITS: SUB-CIRCUITS INTEGRATION

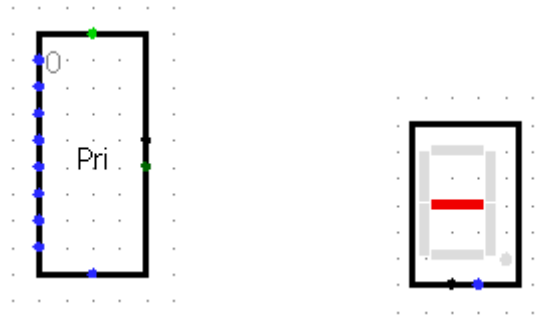


Figure 2. Priority Encoder and Hex Digit Display. The small dots represent different inputs and outputs

PART 2. Subcircuit 2

Design and implement subcircuit 2 using a MUX 4x1 and the necessary logic gates

PART 3. Subcircuit 3

Design and implement subcircuit 3 using a multiplexer MUX 4x1 network and the necessary logic gates

PART 4. Main circuit. Integration

Implement the main circuit using Subcircuits 1, 2 and 3.