

COMPUTER TECHNOLOGY

PRACTICAL SESSION P4 (LOGISIM)

SEQUENTIAL CIRCUITS: FLIP-FLOPs SIMULATION

INTRODUCTION

Flip-Flop and Clock signal in Logisim.

Figure 1 shows flip-flops D and JK in Logisim. Note that asynchronous inputs **Preset** and **Clear** are both active-high inputs. Also note that an active-high **Enable** input appears in both FFs (Enable should be 1).

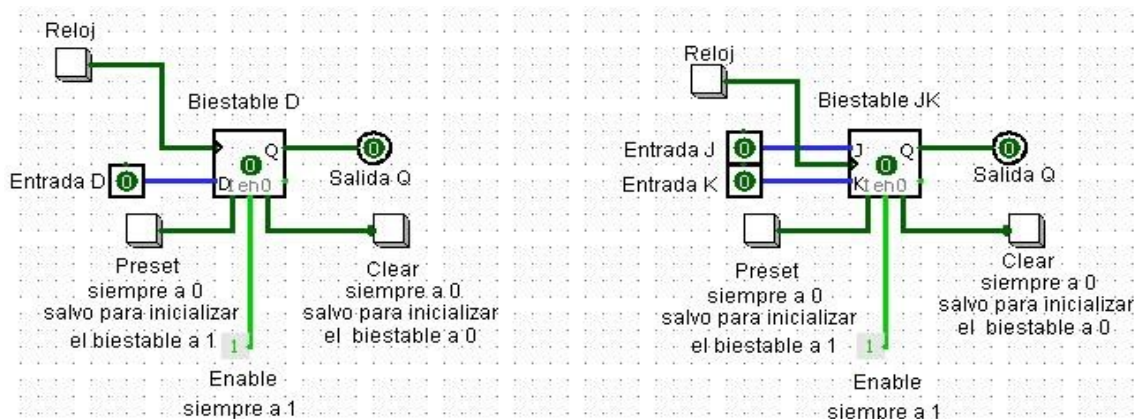




Figure 1

Important remarks:

- To get FFs you have to select **Memory** in the library pane.
- The flip-flops usually have one active-high **Enable** input, so you have to set Enable to 1.
- By default, FFs are positive-edge triggered. Anyway, you can change the trigger as follows. Click in the FF in order to see the attributes panel, choose between *Rising Edge* or *Falling Edge* in the option Trigger.
- The clock signal can be generated by hand by using a single switch or a button. In Part 1, please use a **Button** ( Button in the menu **Input/Output**) as a clock signal. By default, the initial value is 0. Value 1 is generated only at the moment the button is clicked.
- The **Regular Clock Signal** ( Clock) is in the library pane as a part of the **Wiring** menu. Choose Clock. In order to launch the simulation, click **Simulate** and activate *Simulation Enabled*. With the option *Tick Frequency* you can set the clock frequency. If *Ticks Enabled* is activated, the simulation is executed at the chosen frequency. To simulate **cycle by cycle**, disable *Ticks Enabled*. Now, each time you click option *Tick once* or click the clock icon, a half cycle is executed. This method will be used in Part 2 and 3.



COMPUTER TECHNOLOGY

PRACTICAL SESSION P4 (LOGISIM)

SEQUENTIAL CIRCUITS: FLIP-FLOPs SIMULATION

PART 1. INITIALIZATION AND PERFORMANCE OF FFs: D AND JK

Check the functionality of flip-flops JK and D with Logisim.

Flip flop D

INITIALIZATION

Design the circuit of Figure 1 left).

- Select **Memory** in the library pane and get a D FFs
- Connect D to a switch
- Connect the output (Q) to a LED.
- Connect the asynchronous input **Clear** to a **Button** (menu *Input/Output*). Do the same for **Preset**.
- Give a permanent value 1 to **Enable** (use *1-Constante* in menu *Wiring*)
- Connect the **Clock** input to another **Button**.

FUNCTIONALITY

Initialize to 0 the FF, by clicking the **Clear** button. After initializing the flip-flop to 0, the functionality will be checked as follows:

- Set D=1. Click the **Clock** button and check that the next state is 1. Push **Clock** again and again and check that the next state is always 1.
- Set D=0. Click the **Clock** button and check if the next state is 0.

Now, initialize the FF to 1 by pushing once the **Preset** button.

- Set D=0. Click the **Clock** button and check if the next state is 0.
- Set D=1. Click the **Clock** button and check if the next state is 1.

Flip flop JK

INITIALIZATION

Design the circuit of Figure 1 right).

- Select **Memory** in the library pane and get a JK FFs. Click in the FF in order to see the attributes panel and, in the option Trigger, choose *Falling Edge*.
- Connect J and K to two switches.
- Connect the output (Q) to a LED.
- Connect the asynchronous input **Clear** to a **Button** (menu *Input/Output*). Do the same for **Preset**.
- Give a permanent value 1 to **Enable**. Use *1-Constante* in menu *Wiring*
- Connect the **Clock** input to another **Button**.

COMPUTER TECHNOLOGY

PRACTICAL SESSION P4 (LOGISIM)

SEQUENTIAL CIRCUITS: FLIP-FLOPs SIMULATION

FUNCTIONALITY

Initialize the FF to 0 by clicking once the **Clear** button. After initializing the flip-flop to 0, the functionality will be checked as follows:

- Set J=1 and K=0. Click the **Clock** button and check if the next state is 1.
- Set J=0 and K=1. Click the **Clock** button and check if the next state is 0.
- Set J=0 and K=0. Click the **Clock** button and check if the next state is also 0.
- Set J=1 and K=1. Click the **Clock** button and check if the next state is 1. Push the **Clock** button again and again and check that the FF makes changes $0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \dots$


Initialize the FF to 1 by clicking once the **Preset** button. After initializing the flip-flop to 1, the functionality will be checked as follows:

- Set J=0 and K=1. Click the **Clock** button and check if the next state is 0.
- Set J=1 and K=0. Click the **Clock** button and check if the next state is 1.
- Set J=0 and K=0. Click the **Clock** button and check if the next state is also 1.
- Set J=1 and K=1. Click the **Clock** button and check if the next state is 0. Push the **Clock** button again and again and check that the FF makes changes $0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \dots$

PART 2. SIMULATION OF A 2-BITS COUNTER WITH LOGISIM

a) Figure 2 shows a 2-bits upward asynchronous counter composed of two JK flip-flops and an inverter. Implement this circuit in Logisim.

- Step-by-step simulation. First of all, initialize the circuit to 00. For that, use a common **Clear** input (C_D in the figure) as was explained in PART 1. Now, use a **Button** as a common clock signal (CP in the figure). In order to simulate the circuit, click the **Button** again and again and check if the LEDs follow the sequence 01, 10, 11, 00, 01, 10, ... Don't forget to set **Enable** to 1 and choose *rising edge* in both FFs.

- Simulation using a **Regular Clock Signal** ( Clock). Change the **Button** by the **Regular Clock Signal**, initialize the circuit to 00 and simulate the circuit at a frequency of 1Hz .

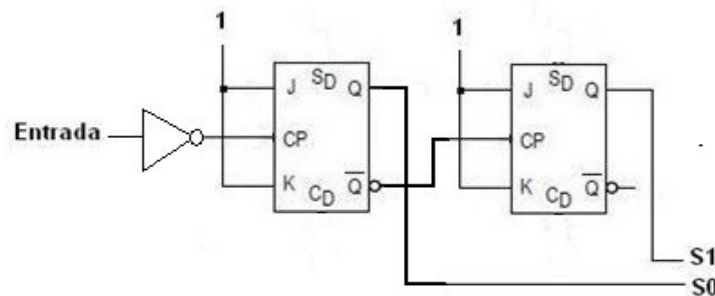


Figure 2.

COMPUTER TECHNOLOGY

PRACTICAL SESSION P4 (LOGISIM)

SEQUENTIAL CIRCUITS: FLIP-FLOPs SIMULATION

- b) Figure 3 shows a 2-bits downward asynchronous counter composed of two JK flip-flops.
- Implement this circuit in Logisim. Initialize now the circuit to 11 by using a common **Preset** input. Choose *rising edge* in both FFs.
 - Simulate the circuit at a frequency of 1Hz. Which is the count now?

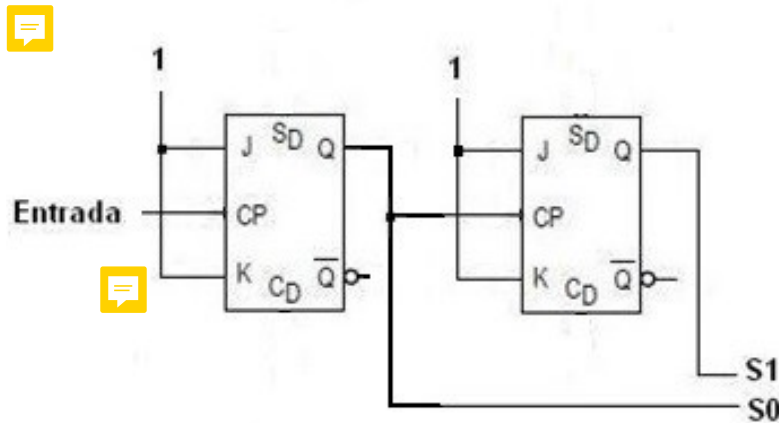


Figure 3

PART 3. IMPLEMENTING A DOUBLE COUNTER

Implement a double counter (main circuit) composed of two subcircuits C1 (2-bits upward asynchronous counter) and C2 (2-bits downward asynchronous counter). The initial counts must be 00 for C1 and 10 for C2. When $C1 = C2$ a yellow LED must be illuminated.

- Use two Hex Digit Displays to see both counts.
- Displays and LEDs can be found in the menu **Input/Output**
- Simulate the circuit at a frequency of 1Hz.

Important remark.

In order to synchronize both counters (simultaneous changes), it is **NECESSARY** to remove the inverter of Figure 2.