

COMPUTER TECHNOLOGY

PRACTICAL SESSION P5 (LOGISIM)

DESIGN OF SEQUENTIAL CIRCUITS



Given the state diagram of Figure 1:

 


Figure 1

Design the sequential circuit using the following flip flops:

- T FF for the most significant flip-flop (T_2).
- D FF for the middle flip-flop (D_1).
- JK FF for the least significant flip-flop (J_0K_0).

Implement T_2 using logic gates, D_1 at the discretion of the student, and J_0K_0 using an active-high output DEC 4x16. The output S must be implemented using a MUX 4x1. Design and simulate the circuit with Logisim.

Check that if $x=0$ the state sequence is:

$q_0 \rightarrow q_5 \rightarrow q_3 \rightarrow q_4 \rightarrow q_2 \rightarrow q_1 \rightarrow q_0$

Check that if $x=1$ the state sequence is:

$q_0 \rightarrow q_1 \rightarrow q_4 \rightarrow q_3 \rightarrow q_5 \rightarrow q_2 \rightarrow q_0$

COMPUTER TECHNOLOGY

PRACTICAL SESSION P5 (LOGISIM)

DESIGN OF SEQUENTIAL CIRCUITS

REMARK 1: The state encoding is shown in Table 1.

	Q_2	Q_1	Q_0
q_0	0	0	0
q_1	0	0	1
q_2	0	1	0
q_3	0	1	1
q_4	1	0	0
q_5	1	0	1

Table 1

REMARK 2: The state of the circuit must be visualized using 3 orange LEDs and a display (take *Hex Digit Display*), corresponding to the outputs of the three flip-flops. These LEDs must be placed horizontally, in the following order: $Q_2Q_1Q_0$. The output S must be visualized using a green LED.

FILL OUT THE TABLE BELOW:

E	$Q_2(t)$	$Q_1(t)$	$Q_0(t)$	$Q_2(t+1)$	$Q_1(t+1)$	$Q_0(t+1)$	T_2	D_1	J_0	K_0	S
0	0	0	0	1	0	1	1	0	1	X	1
0	0	0	1	0	0	0	0	0	X	1	1
0	0	1	0	0	0	1	0	0	1	X	0
0	0	1	1	1	0	0	1	0	X	1	0
0	1	0	0	0	0	1	1	0	0	X	0
0	1	0	1	0	1	1	1	1	X	0	0
0	1	1	0	X	X	X	X	X	X	X	X
0	1	1	1	X	X	X	X	X	X	X	X
1	0	0	0	0	0	1	0	0	1	X	0
1	0	0	1	0	0	0	1	0	X	1	1
1	0	1	0	0	0	0	0	0	0	X	1
1	0	1	1	0	0	1	1	0	X	0	1
1	1	0	0	1	1	1	1	1	1	X	1
1	1	0	1	1	1	0	1	1	X	1	0
1	1	1	0	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X

